

## PROJECT A SUBMISSION



**Program: Computer Engineering and  
Software Systems**

**Course Code: CSE111**

**Course Name: Digital Design**

**Examination Committee**

**Dr. Manal Mohsen**

**Ain Shams University  
Faculty of Engineering  
Spring Semester – 2022**

**May 28, 2022**



## **Students Personal Information**

<b>Student Name:</b>	Yousef Emad Eldin Elshahat
<b>Student Code:</b>	20P3844
<b>Student Name:</b>	Ahmed aboBakr Hafez
<b>Student Code:</b>	20P4588
<b>Student Name:</b>	Mohamed Sohail Sayed Ibrahim
<b>Student Code:</b>	20P3576



## Table of Contents

<b>1.0 Project Description .....</b>	<b>4</b>
<b>2.0 Project Requirements .....</b>	<b>4</b>
<b>3.0 Equipments Used .....</b>	<b>4</b>
<b>4.0 Comparator .....</b>	<b>5</b>
Truth Table: .....	5
Kmaps: .....	5
Simulation: .....	6
<b>5.0 Lock LED .....</b>	<b>7</b>
Truth Table: .....	7
Kmaps: .....	7
Simulation: .....	7
<b>6.0 Flip Flops .....</b>	<b>8</b>
Truth Table: .....	8
Kmaps: .....	8
<b>7.0 Final Result .....</b>	<b>9</b>
Simulation: .....	9
Implementation: .....	10
Videos while circuit working: .....	10



## 1.0 Project Description:

The objective is to design and implement a digital circuit that acts like a digital lock for a safe which accepts a binary passcode, compare it to a preset code by a comparator and takes an action depending on the validity of the entered value. If a wrong code is entered for three successive trials, the lock should no longer accept a new value unless a Reset switch is pressed.

## 2.0 Project Requirements:

1. A 3-bit binary passcode is entered through switches (Preferably dipswitches for ease of use). The preset code is also adjusted through dipswitches.
2. A switch is used to pass the input to the comparator via flip flops.
3. Wrong trials counter is incremented each time a code is passed and a false indication is given by the comparator. Ready-made counter IC could be used.
4. Output action is to illuminate a green LED in case of correct code or a red LED otherwise and another output LED is to be illuminated when wrong trials counter reaches three

## 3.0 Equipments Used:

(2) Dip Switch	(4 inputs )
(5) D-flipflop	(IC 7474 )
(1) 2-input Xnor	(IC 74266)
(1) 3-input Nand	(IC 7411 )
(1) Inverter	(IC 7404 )
(1) And	(IC 7408 )
(1) OR	(IC 7432 )
(1) NOR	(IC 7402 )
(2) Push Button	
(7) Resistance	( 1k $\Omega$ )
(3) LEDs	
Male-Male wires	
Power supply(5v)	



## 4.0 Comparator:

Truth Table:

Password =  $A_0 A_1 A_2$

Input =  $B_0 B_1 B_2$

$A_0$	$B_0$	$F1$
0	0	1
0	1	0
1	0	0
1	1	1

$A1$	$B1$	$F2$
0	0	1
0	1	0
1	0	0
1	1	1

$A2$	$B2$	$F3$
0	0	1
0	1	0
1	0	0
1	1	1

$F1$	$F2$	$F3$	$F$
1	1	1	1
0	0	0	0
0	0	0	0
1	1	1	1

Kmaps:

	$B_0'$	$B_0$
$A_0'$	1	0
$A_0$	0	1

	$B1'$	$B1$
$A1'$	1	0
$A1$	0	1

	$B2'$	$B2$
$A2'$	1	0
$A2$	0	1

$$F1 = A_0' B_0' + A_0 B_0$$

$$F2 = A_1' B_1' + A_1 B_1$$


$$F3 = A_2' B_2' + A_2 B_2$$

	$F2'$		$F2$	
$F1'$	0	0	1	0
$F1$	0	0	1	0
	$F3'$		$F3$	

$$F = F1 F2 F3$$



Simulation:

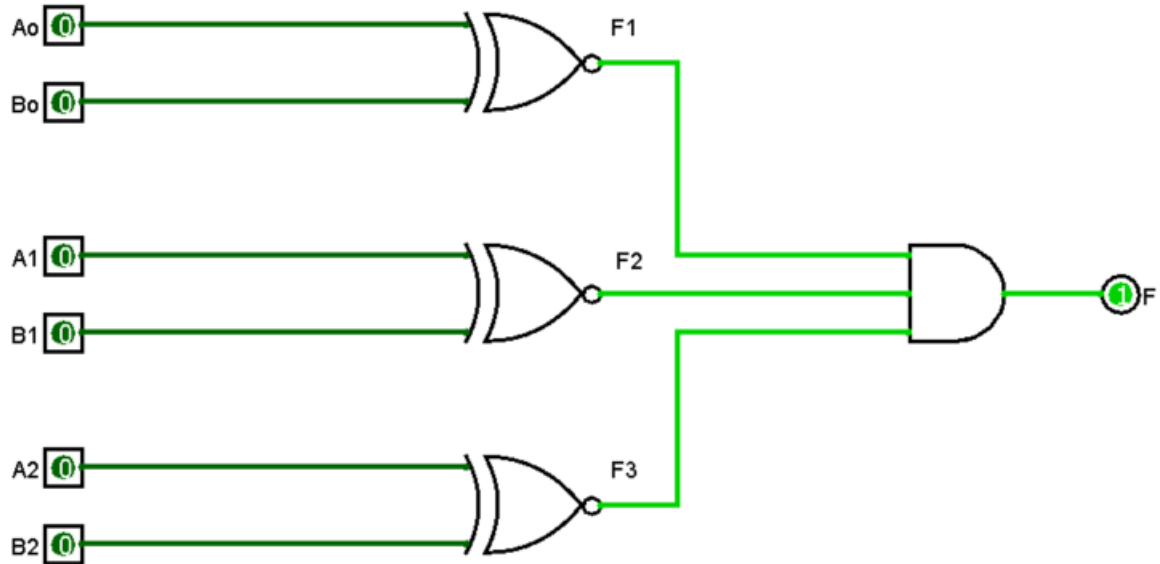



## 5.0 Lock LED:

Truth Table:

X	A	A <sup>+</sup>	Y	D <sub>A</sub>
0	0	0	0	0
0	1	1	1	1
1	0	1	1	1
1	1	1	1	1


Kmap:

	A <sup>'</sup>	A
X <sup>'</sup>	0	1
X	1	1

$$D_A = A + X$$


$$y = A + X$$

Simulation:

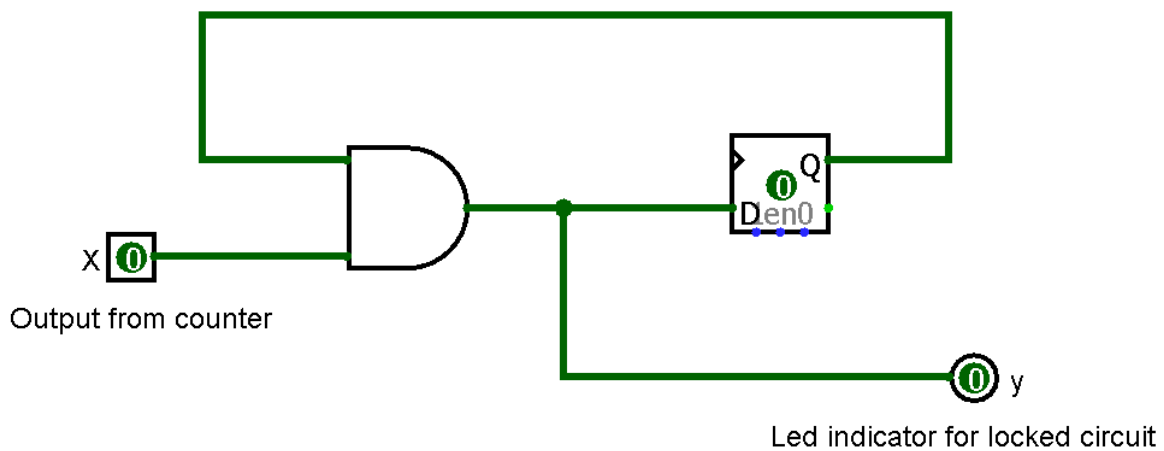



## 6.0 Flip Flops:

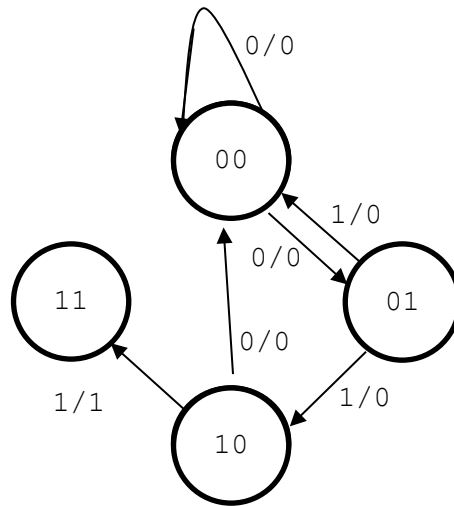

Truth Table:

X	A	B	A <sup>+</sup>	B <sup>+</sup>	D <sub>A</sub>	D <sub>B</sub>	y
0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0
0	1	0	0	0	0	0	0
0	1	1	0	0	0	0	0
1	0	0	0	1	0	1	0
1	0	1	1	0	1	0	0
1	1	0	1	1	1	1	1
1	1	1	x	x	x	x	x

Kmap:

	A'		A	
X'	0	0	0	0
X	0	1	x	1
	B'	B	B'	B

$$D_A = XA + XB$$

	A'		A	
X'	0	0	0	0
X	1	0	x	1
	B'	B	B'	B

$$D_B = XB'$$


	A'		A	
X'	0	0	0	0
X	0	0	x	1
	B'	B	B'	B

$$y = XA$$




## 7.0 Final Result:

Simulation:

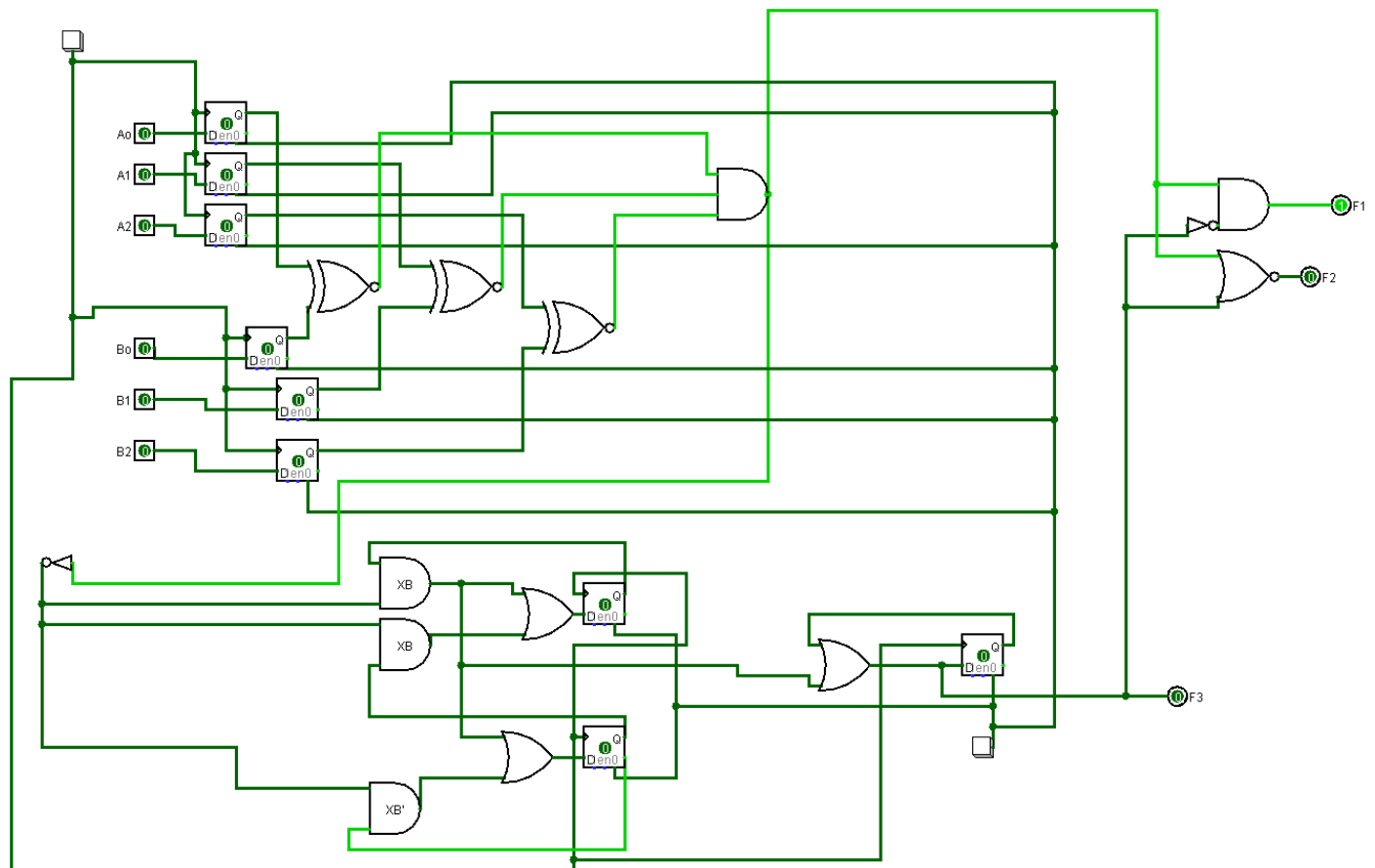

## Implementation:

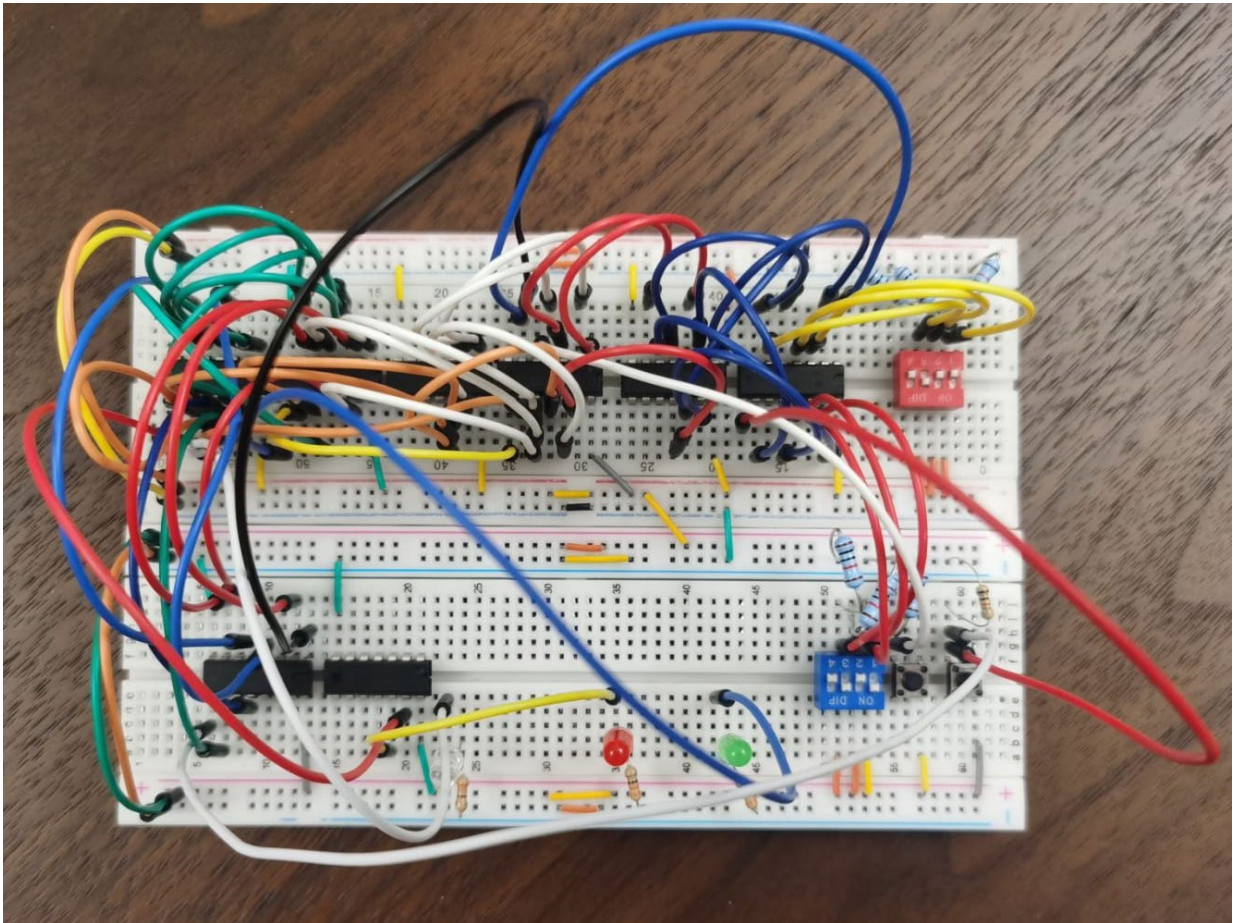

Videos while circuit working:

<https://drive.google.com/drive/folders/1zgUDWRA3RxaD7G7DkqcJwamPcUiSnO4s?usp=sharing>